

# C5-Supplementary Information


Repeat Example 5.1 using the ideal op amp model.

## Practice Problem 5.2

**Answer:**  $-2,200 \mu\text{A}$ .

### Example 5.1

A 741 op amp has an open-loop voltage gain of  $2 \times 10^5$ , input resistance of  $2 \text{ M}\Omega$ , and output resistance of  $50 \Omega$ . The op amp is used in the circuit of Fig. 5.6(a). Find the closed-loop gain  $v_o/v_s$ . Determine current  $i$  when  $v_s = 2 \text{ V}$ .

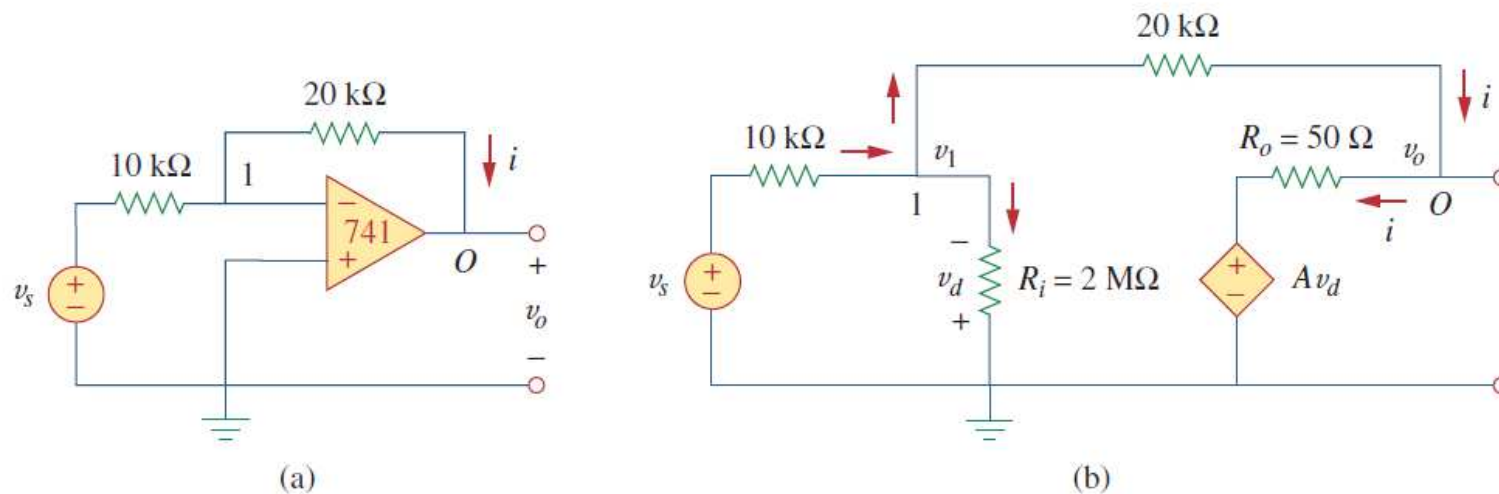


**Figure 5.6**

For Example 5.1: (a) original circuit, (b) the equivalent circuit.

# Example 5.1

## Example 5.1

A 741 op amp has an open-loop voltage gain of  $2 \times 10^5$ , input resistance of  $2 \text{ M}\Omega$ , and output resistance of  $50 \Omega$ . The op amp is used in the circuit of Fig. 5.6(a). Find the closed-loop gain  $v_o/v_s$ . Determine current  $i$  when  $v_s = 2 \text{ V}$ .

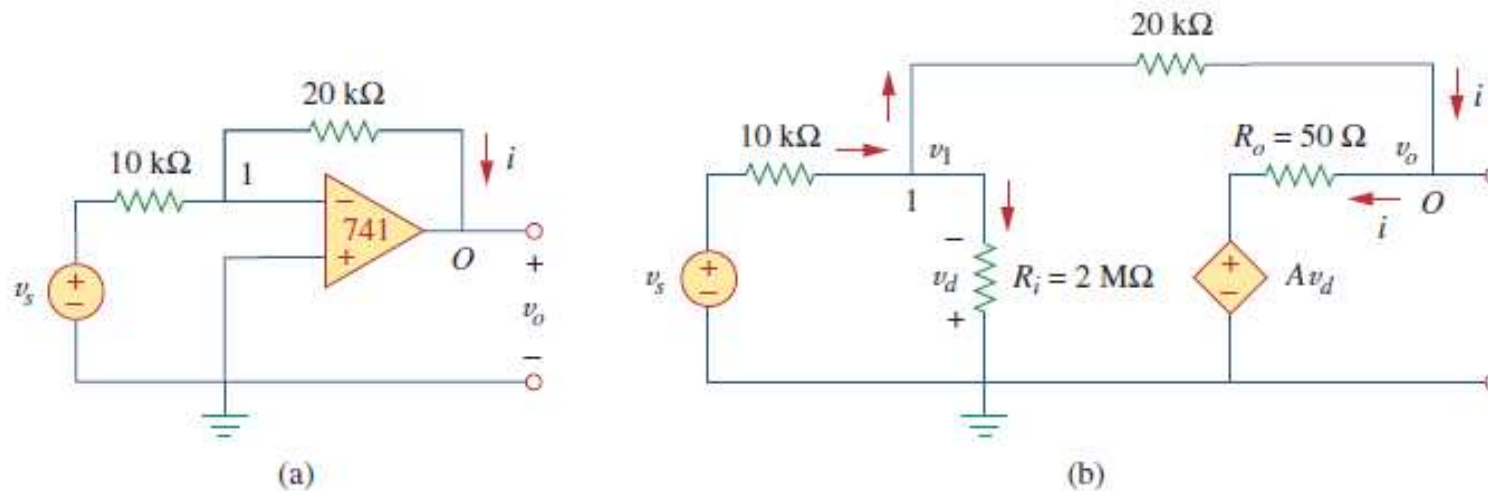


**Figure 5.6**

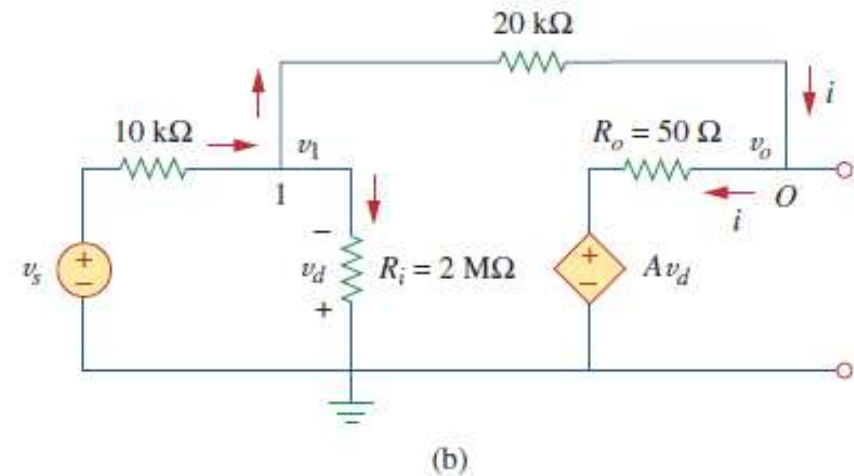For Example 5.1: (a) original circuit, (b) the equivalent circuit.

**A real op amp**

- 1. The equivalent circuit



- 2. KCL@node 1

$$\frac{v_s - v_1}{10 \times 10^3} = \frac{v_1}{2000 \times 10^3} + \frac{v_1 - v_o}{20 \times 10^3}$$

$$200v_s = 301v_1 - 100v_o$$

$$2v_s = 3v_1 - v_o \quad \Rightarrow \quad v_1 = \frac{2v_s + v_o}{3} \quad (5.1.1)$$

- 3. KCL@node O

$$\frac{v_1 - v_o}{20 \times 10^3} = \frac{v_o - Av_d}{50}$$



$$v_d = -v_1 \text{ and } A = 200,000$$

$$v_1 - v_o = 400(v_o + 200,000v_1) \quad (5.1.2)$$

- 4.

- 3 unknowns ( $v_s, v_1, v_o$ ); need to get relation between  $v_s$  and  $v_o \rightarrow$  eliminate  $v_1$
- Substitute Eq. (5.1.2) into Eq. (5.1.1)


$$0 \approx 26,667,067v_o + 53,333,333v_s \Rightarrow \frac{v_o}{v_s} = -1.9999699$$

This is closed-loop gain, because the 20-k feedback resistor closes the loop between the output and input terminals.

- 5.

- When  $v_s=2V$ ,  $v_o=-3.9999398V$ .
- From Eq. (5.1.1), we obtain  $v_1=20.066667 \mu V$ .
- Thus,  $i = \frac{v_1 - v_o}{20 \times 10^3} = 0.19999 \text{ mA}$

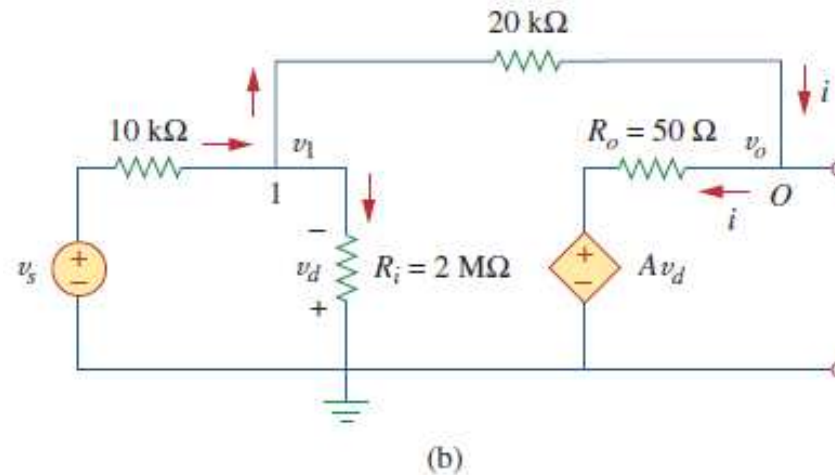- Question: What if there is no feedback loop?



- Answer:

- $v_1 = v_s \times (2/0.01 + 2)$

- E.g., for  $v_s = 2V$ ,  $v_1 \cong 2V$ ,

$$|v_o| = |A v_d| \gg |V_{cc}|, \text{ in saturation region}$$


The feedback loop is helpful to operate an op amp in linear region.

# Problem 5.2

Repeat Example 5.1 using the ideal op amp model.

## Practice Problem 5.2

**Answer:**  $-2, 200 \mu\text{A}$ .

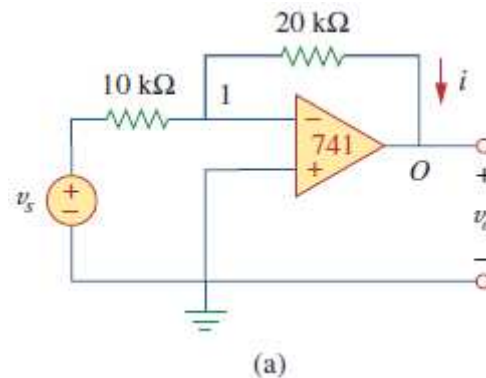

$$V_1 = 0\text{V}$$

$$(v_s - 0)/10\text{k} = (0 - V_o)/20\text{k}$$

$$V_o/V_s = -2$$

$$\text{For } V_s = 2\text{V}, V_o = -4\text{V}$$

$$i = (0 + 4)/20\text{k} = 200\mu\text{A}$$

# Comparisons

	Real op amp	Ideal op amp
Gain $v_o/v_s$	-1.9999699	-2
$v_1$	20.066667 $\mu\text{V}$	0 V
$v_o$	-3.9999398V $\mu\text{V}$	-4V
$i$	199.999 $\mu\text{A}$	200 $\mu\text{A}$
$i_{R_o}$ (i through $R_o$ )	199.999 $\mu\text{A}$	200 $\mu\text{A}$
$v_d = 0 - v_1$	-20.066667 $\mu\text{V}$	0V
$A v_d$	-4.0133 V	$v_o - i_{R_o} \times R_o = -4\text{V} \neq 0$ *

\* cannot be calculated by  $A \times v_d$  since  $\infty \times 0$  is not defined.